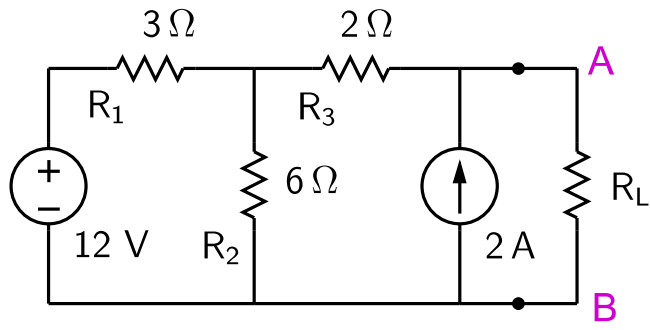




Maximum power transfer: example

Find R_L for which P_L is maximum.





Maximum power transfer: example

Find R_L for which P_L is maximum.

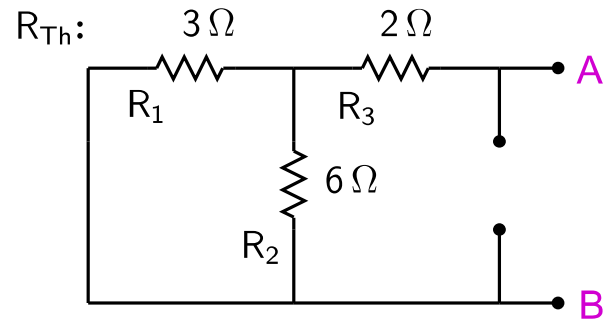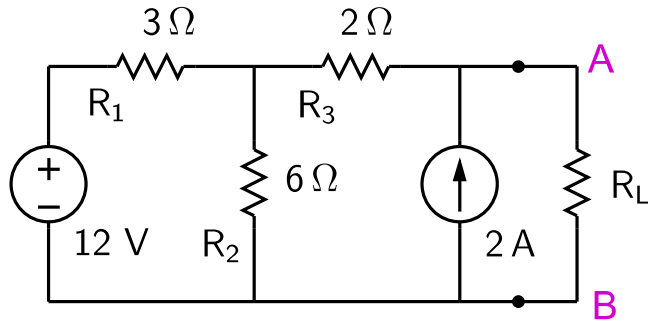

Maximum power transfer: example

Find R_L for which P_L is maximum.

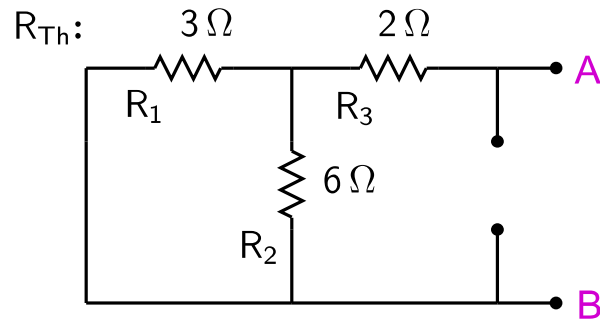
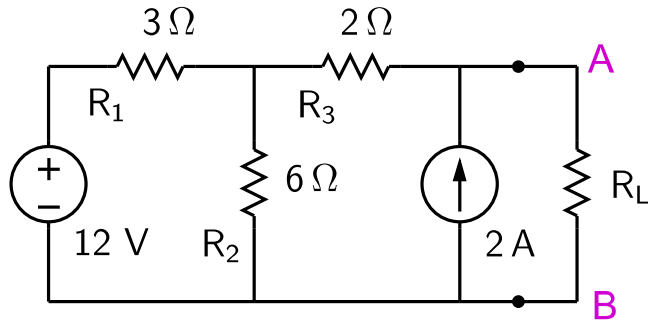


$$R_{Th} = (R_1 \parallel R_2) + R_3 = (3 \parallel 6) + 2$$


$$= 3 \times \left(\frac{1 \times 2}{1 + 2} \right) + 2 = 4\ \Omega$$

Maximum power transfer: example

Find R_L for which P_L is maximum.

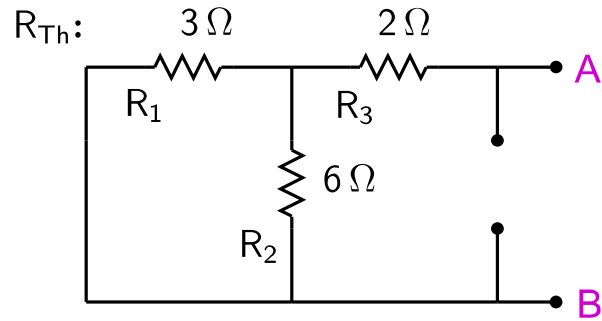
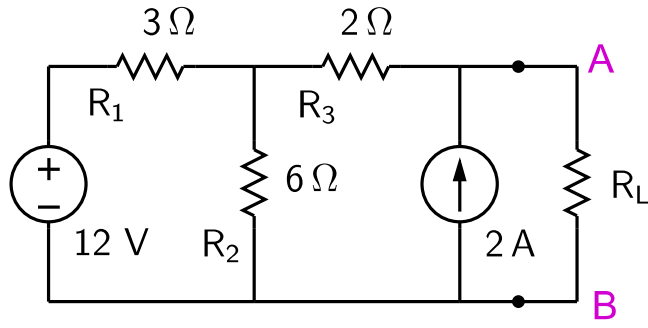

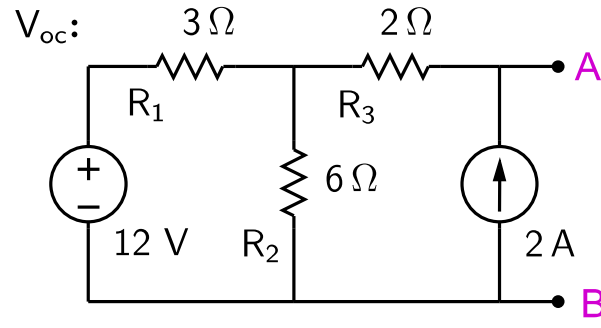
$$\begin{aligned} R_{Th} &= (R_1 \parallel R_2) + R_3 = (3 \parallel 6) + 2 \\ &= 3 \times \left(\frac{1 \times 2}{1 + 2} \right) + 2 = 4\ \Omega \end{aligned}$$




Maximum power transfer: example



Find R_L for which P_L is maximum.

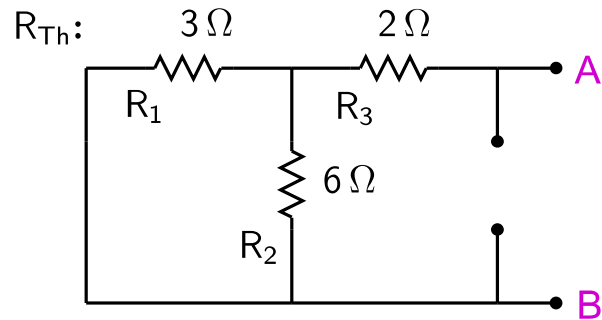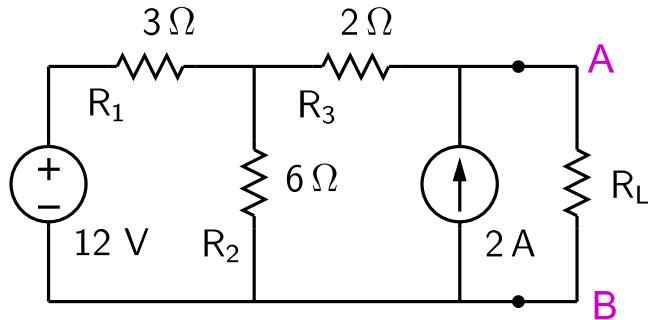
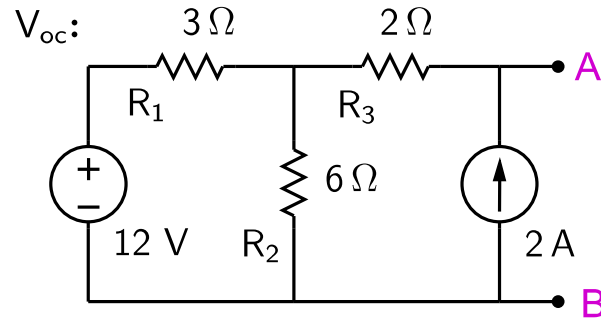
$$\begin{aligned} R_{Th} &= (R_1 \parallel R_2) + R_3 = (3 \parallel 6) + 2 \\ &= 3 \times \left(\frac{1 \times 2}{1 + 2} \right) + 2 = 4\ \Omega \end{aligned}$$





Use superposition to find V_{oc} :

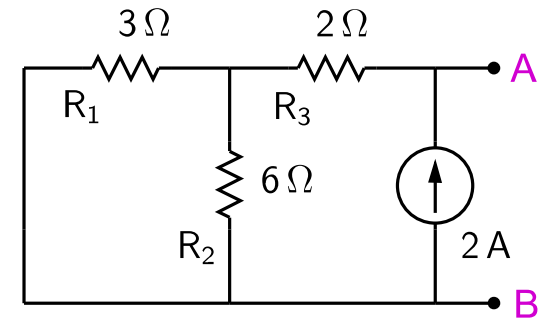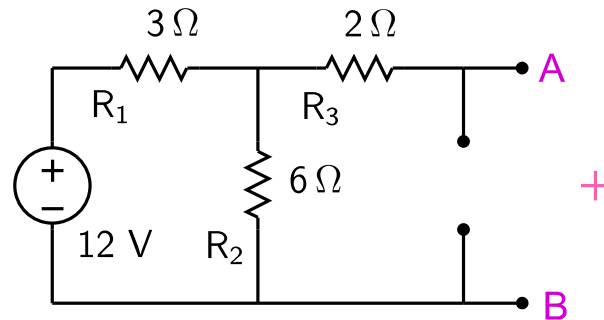


Maximum power transfer: example



Find R_L for which P_L is maximum.

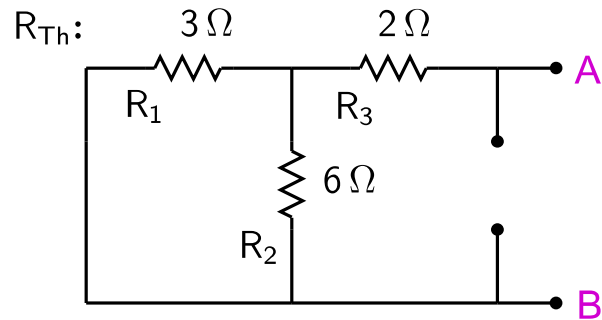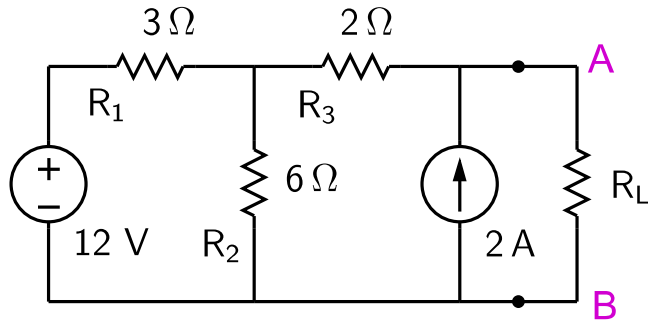
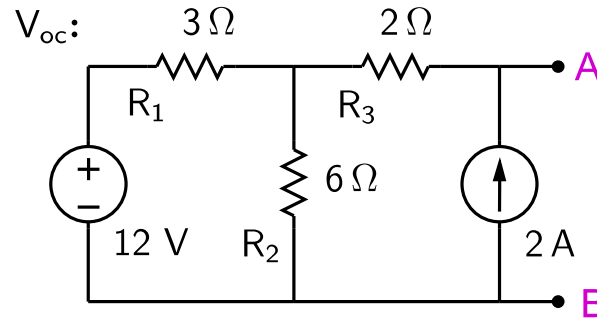
$$\begin{aligned} R_{Th} &= (R_1 \parallel R_2) + R_3 = (3 \parallel 6) + 2 \\ &= 3 \times \left(\frac{1 \times 2}{1 + 2} \right) + 2 = 4\ \Omega \end{aligned}$$





Use superposition to find V_{oc} :

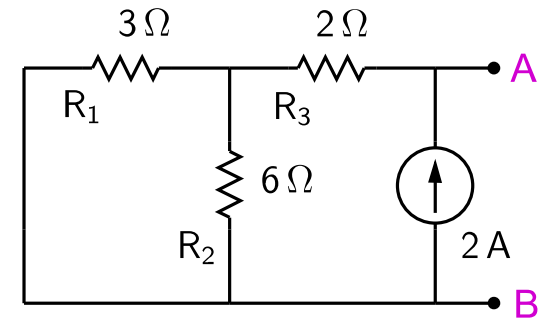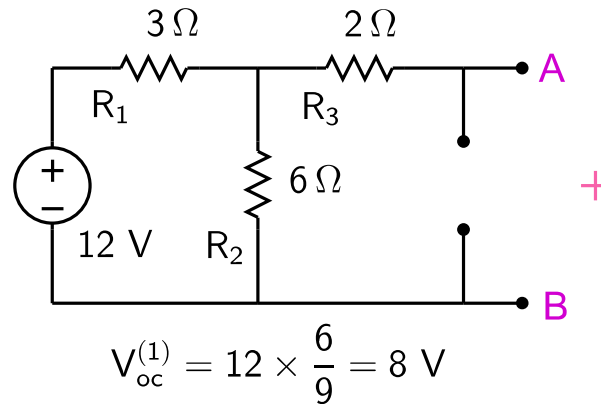


Maximum power transfer: example



Find R_L for which P_L is maximum.

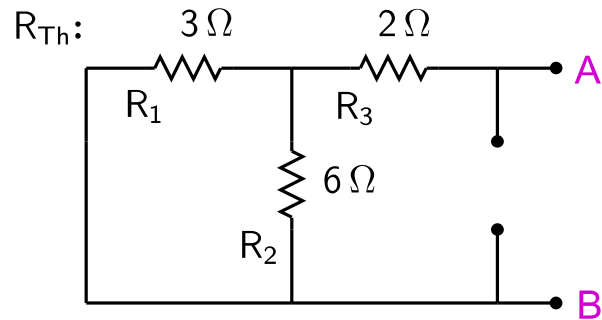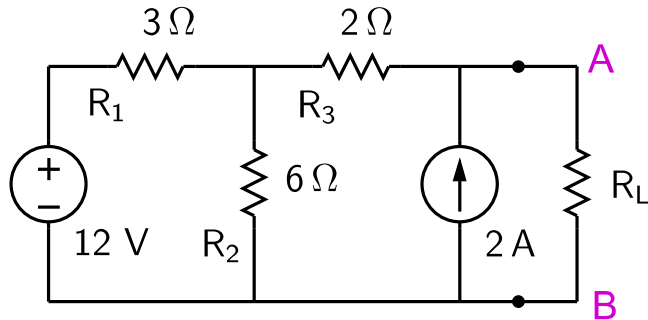
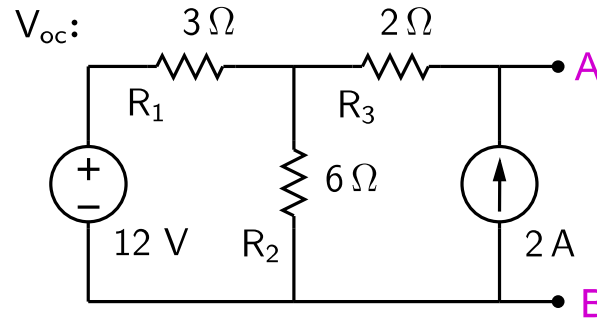
$$\begin{aligned} R_{Th} &= (R_1 \parallel R_2) + R_3 = (3 \parallel 6) + 2 \\ &= 3 \times \left(\frac{1 \times 2}{1 + 2} \right) + 2 = 4\ \Omega \end{aligned}$$





Use superposition to find V_{oc} :

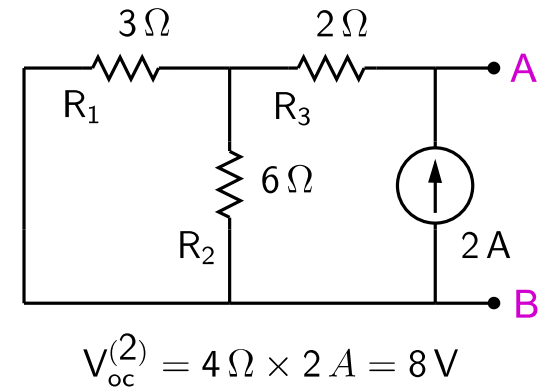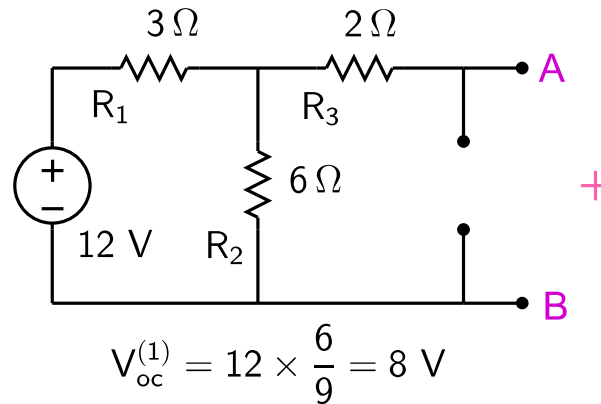


Maximum power transfer: example


Find R_L for which P_L is maximum.

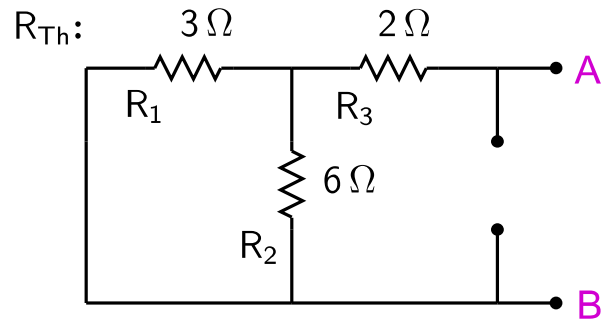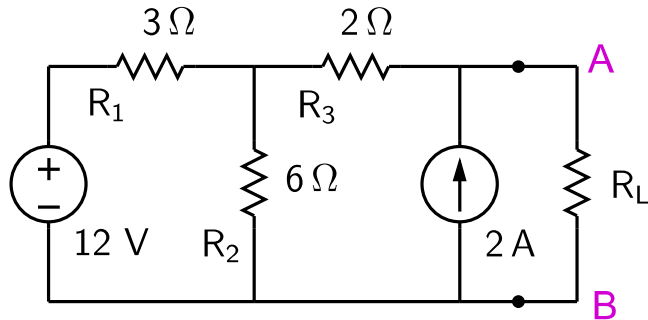

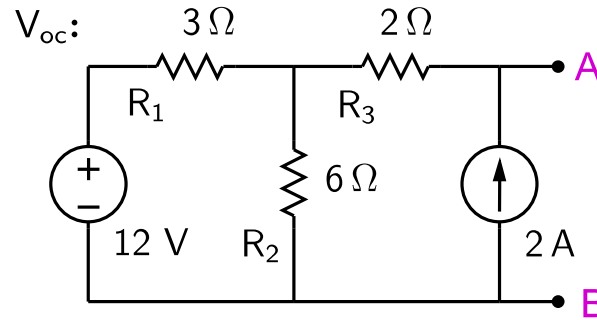
$$\begin{aligned} R_{Th} &= (R_1 \parallel R_2) + R_3 = (3 \parallel 6) + 2 \\ &= 3 \times \left(\frac{1 \times 2}{1 + 2} \right) + 2 = 4\ \Omega \end{aligned}$$



Use superposition to find V_{oc} :

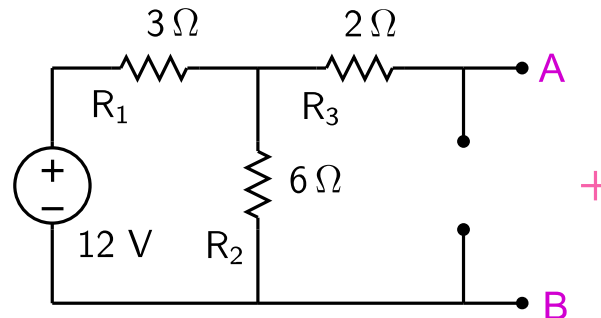


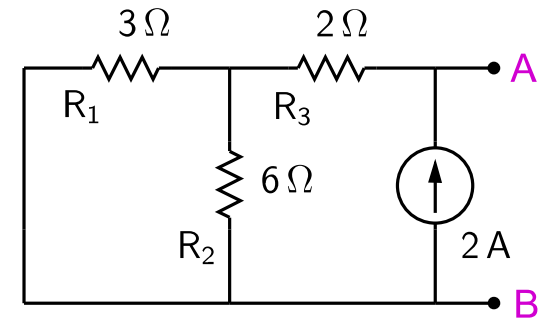
$$V_{oc}^{(1)} = 12 \times \frac{6}{9} = 8\ \text{V}$$



$$V_{oc} = V_{oc}^{(1)} + V_{oc}^{(2)} = 8 + 8 = 16\ \text{V}$$


Maximum power transfer: example

Find R_L for which P_L is maximum.

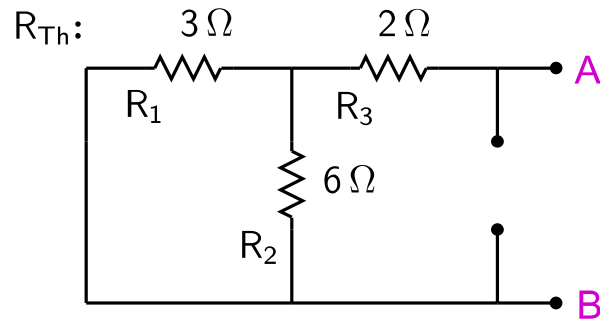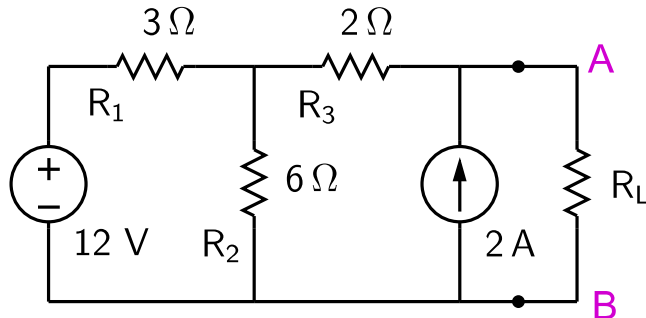


$$R_{Th} = (R_1 \parallel R_2) + R_3 = (3 \parallel 6) + 2$$

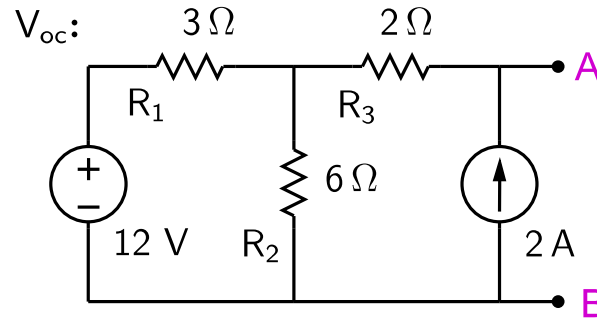
$$= 3 \times \left(\frac{1 \times 2}{1 + 2} \right) + 2 = 4 \Omega$$



Use superposition to find V_{oc} :

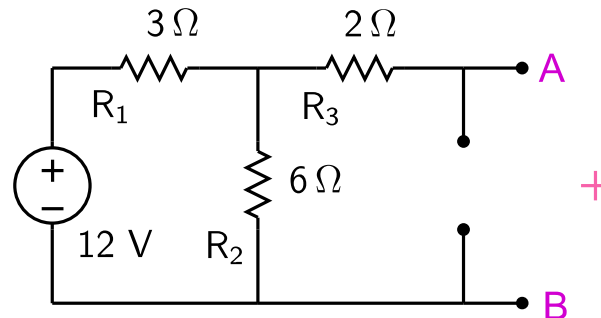

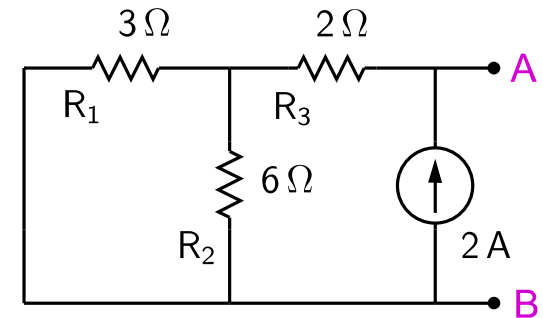
$$V_{oc}^{(1)} = 12 \times \frac{6}{9} = 8 \text{ V}$$



$$V_{oc}^{(2)} = 4 \Omega \times 2 \text{ A} = 8 \text{ V}$$
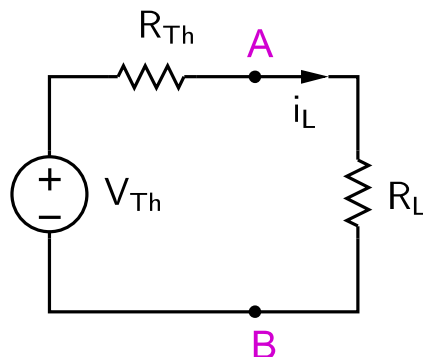
$$V_{oc} = V_{oc}^{(1)} + V_{oc}^{(2)} = 8 + 8 = 16 \text{ V}$$




P_L is maximum when $R_L = R_{Th} = 4 \Omega$


$$\Rightarrow i_L = V_{Th} / (2 R_{Th}) = 2 \text{ A}$$

$$P_L^{\max} = 2^2 \times 4 = 16 \text{ W}.$$


Thevenin's theorem: example

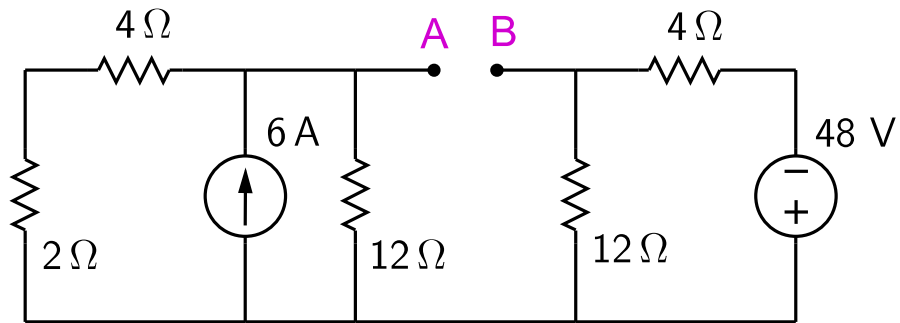


Thevenin's theorem: example

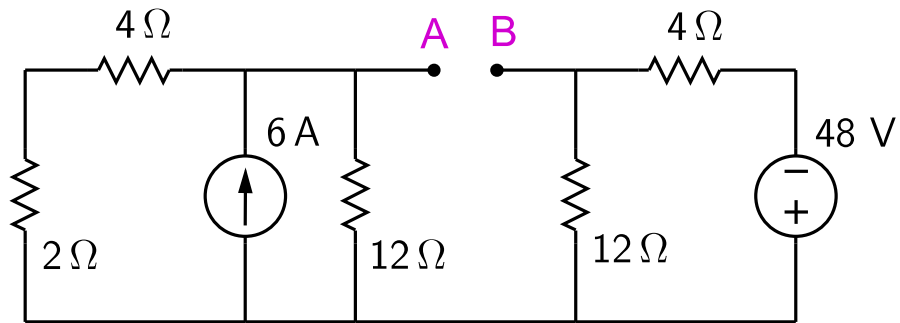



R_{Th} :

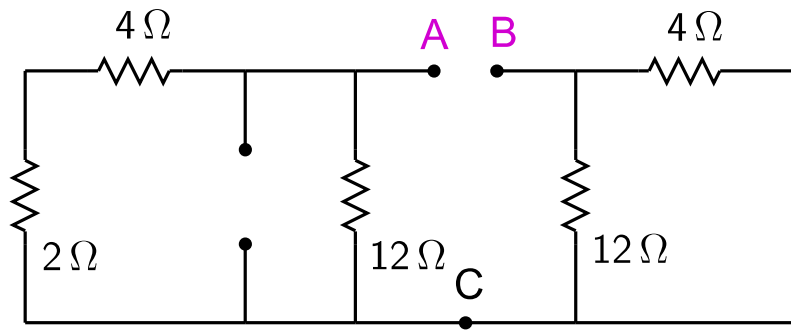


Thevenin's theorem: example

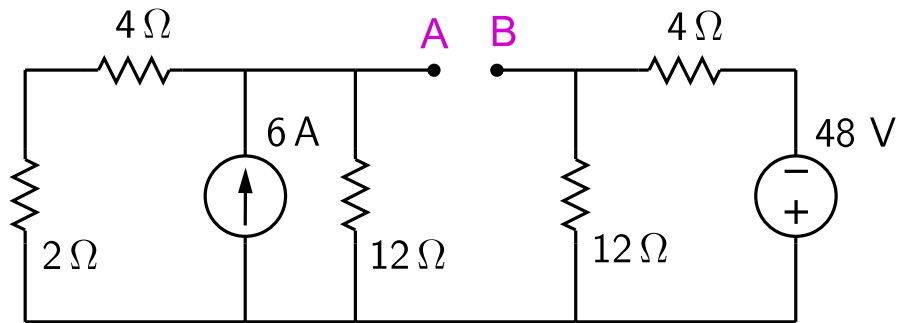



R_{Th} :

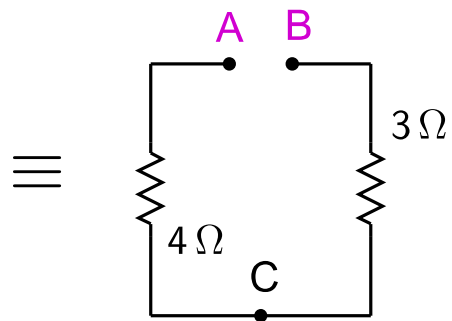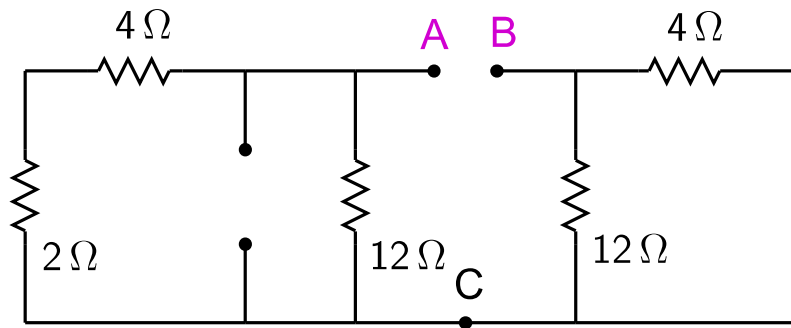


Thevenin's theorem: example

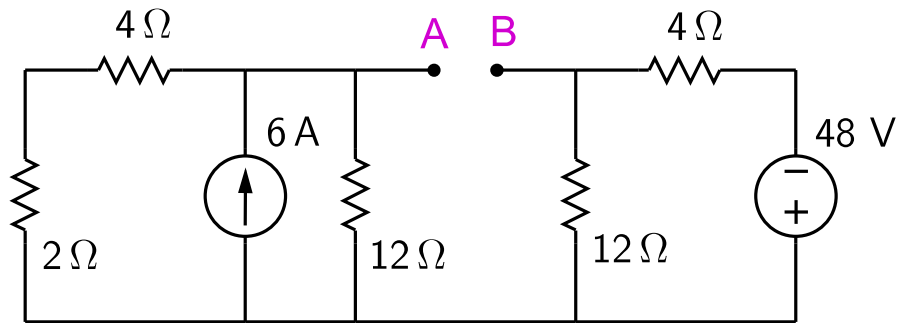



R_{Th} :

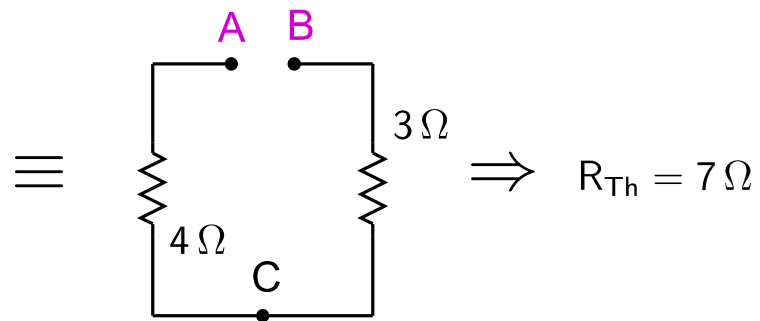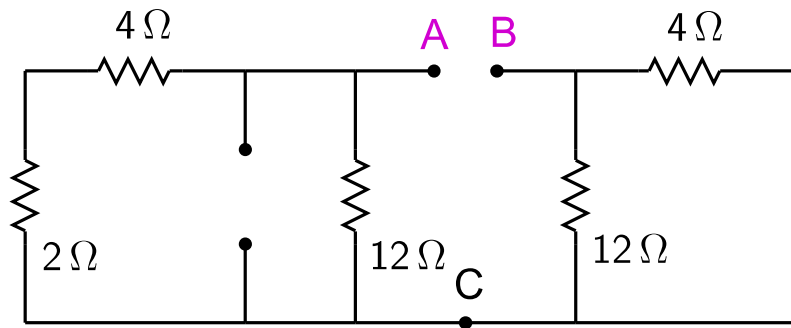


Thevenin's theorem: example

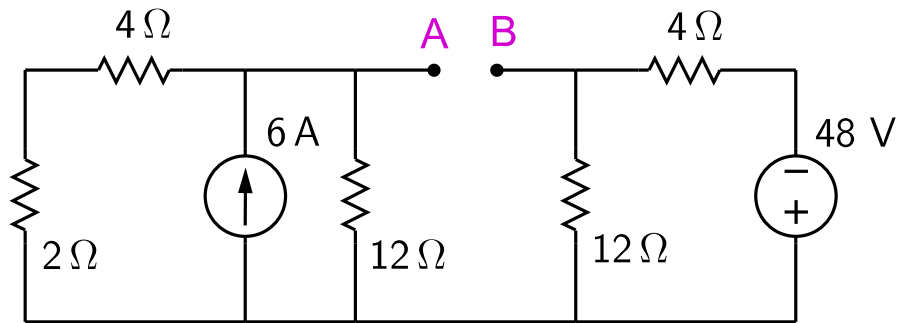


R_{Th} :

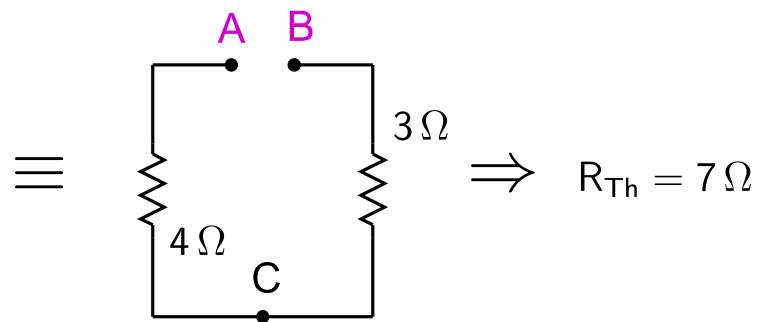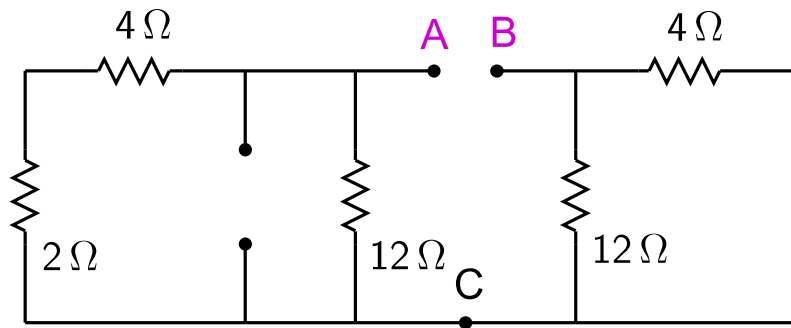



V_{oc} :

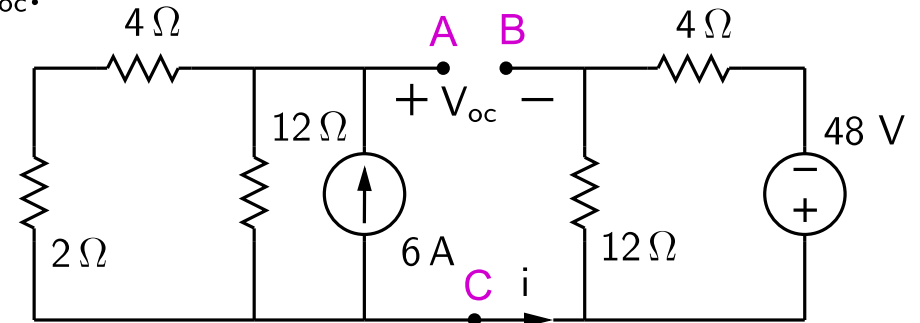


Thevenin's theorem: example

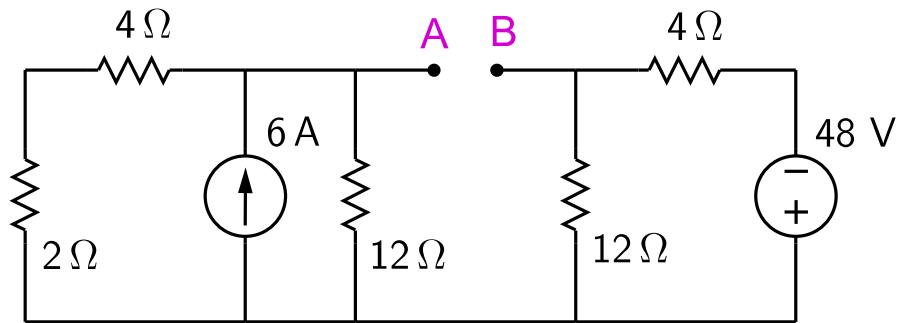

R_{Th} :

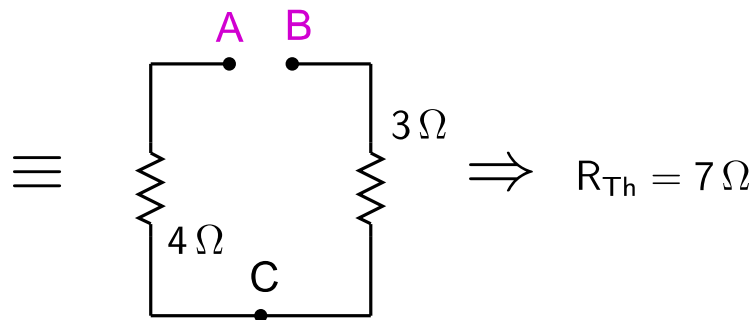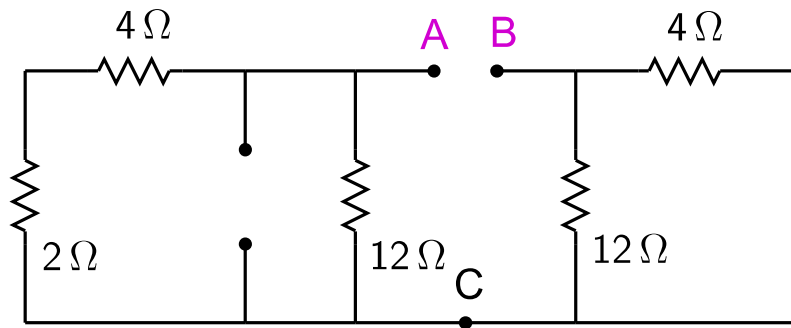


V_{oc} :

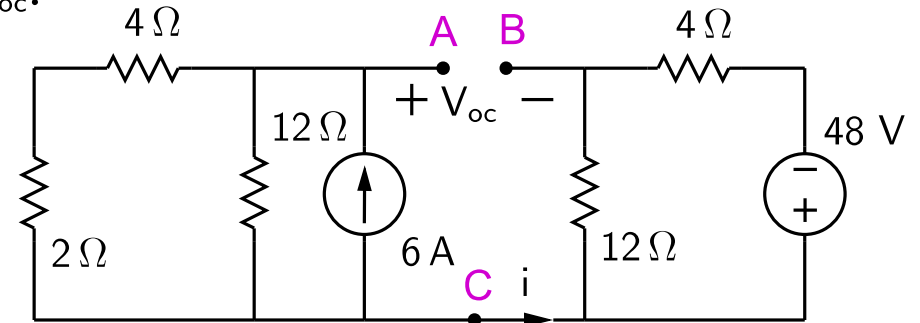



Note: $i = 0$ (since there is no return path).

$$\begin{aligned}
 V_{AB} &= V_A - V_B \\
 &= (V_A - V_C) + (V_C - V_B) \\
 &= V_{AC} + V_{CB} \\
 &= 24\text{ V} + 36\text{ V} = 60\text{ V}
 \end{aligned}$$


Thevenin's theorem: example

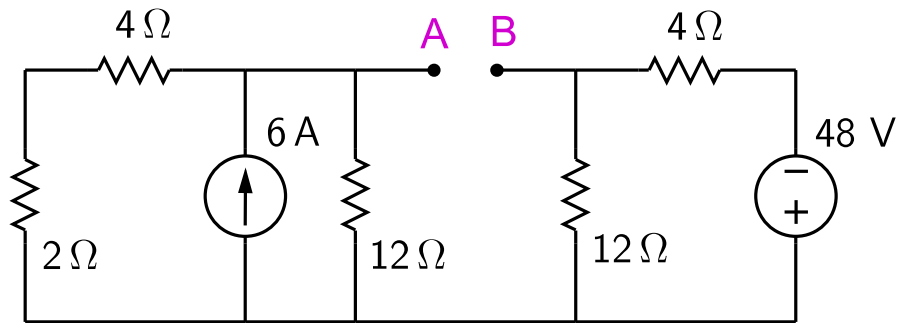

R_{Th} :

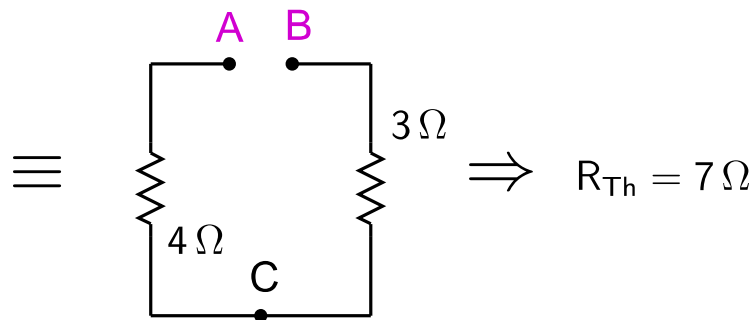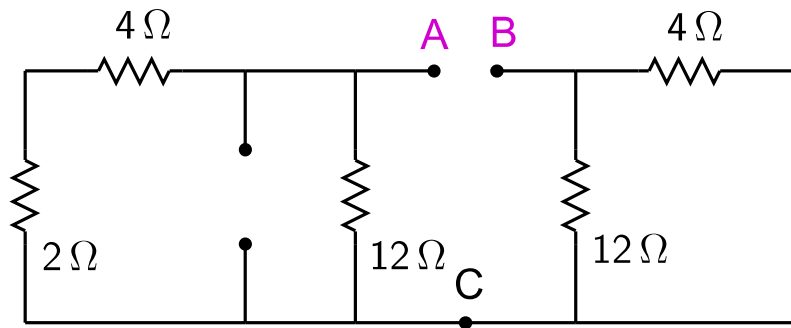

V_{oc} :

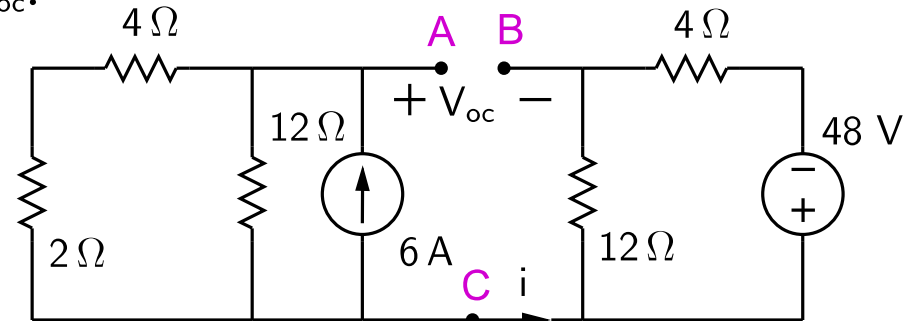


Note: $i = 0$ (since there is no return path).

$$\begin{aligned} V_{AB} &= V_A - V_B \\ &= (V_A - V_C) + (V_C - V_B) \\ &= V_{AC} + V_{CB} \\ &= 24\text{ V} + 36\text{ V} = 60\text{ V} \end{aligned}$$



$$V_{Th} = 60\text{ V}$$

$$R_{Th} = 7\ \Omega$$


Thevenin's theorem: example

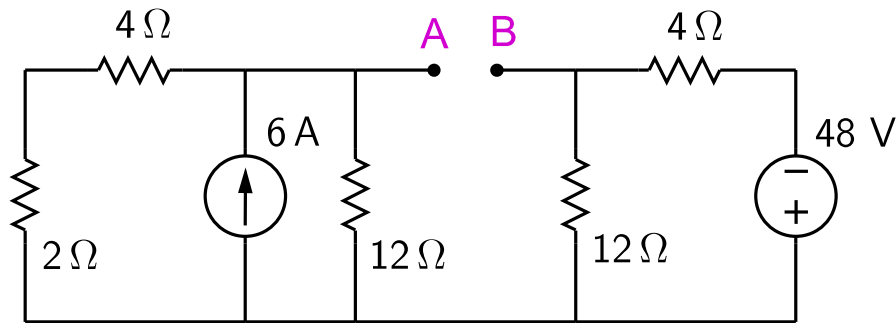

R_{Th} :

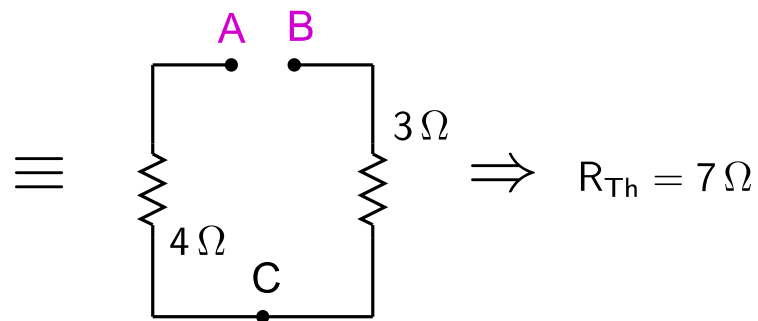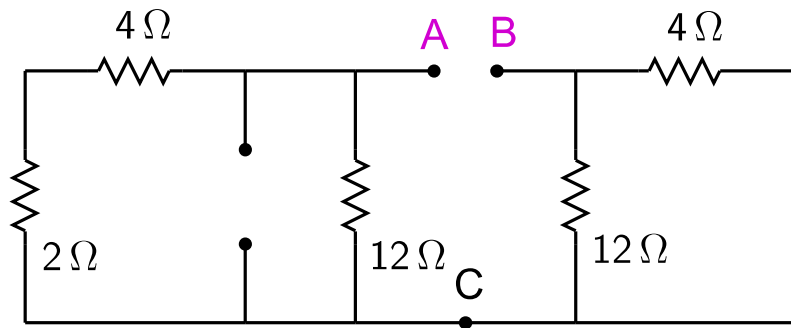


V_{oc} :

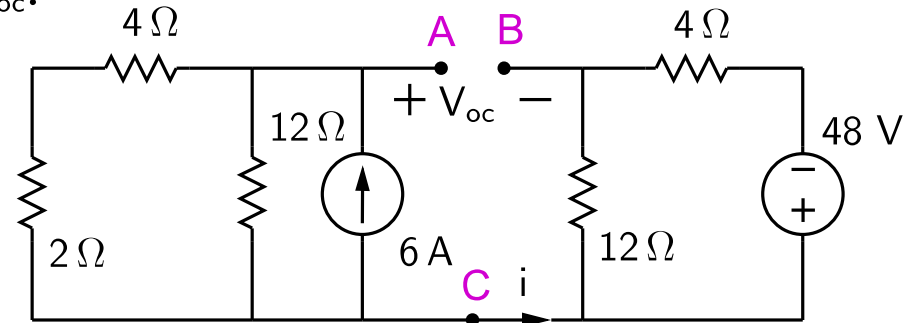

Note: $i = 0$ (since there is no return path).


$$\begin{aligned} V_{AB} &= V_A - V_B \\ &= (V_A - V_C) + (V_C - V_B) \\ &= V_{AC} + V_{CB} \\ &= 24 \text{ V} + 36 \text{ V} = 60 \text{ V} \end{aligned}$$
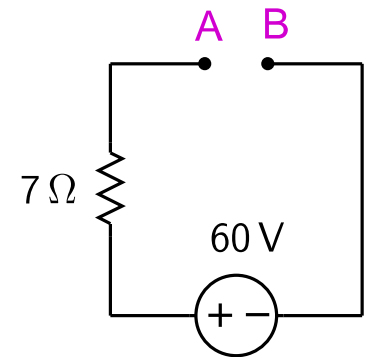
$$\begin{aligned} V_{Th} &= 60 \text{ V} \\ R_{Th} &= 7 \Omega \end{aligned}$$




Graphical method for finding V_{Th} and R_{Th}

SEQUEL file: ee101_thevenin_1.sqproj

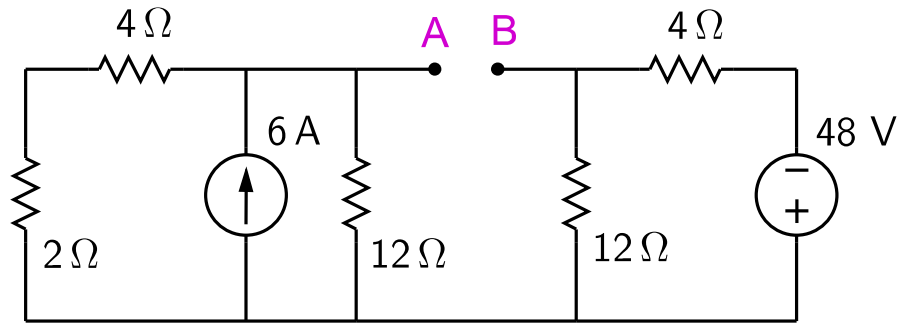


Graphical method for finding V_{Th} and R_{Th}

SEQUEL file: ee101_thevenin_1.sqproj

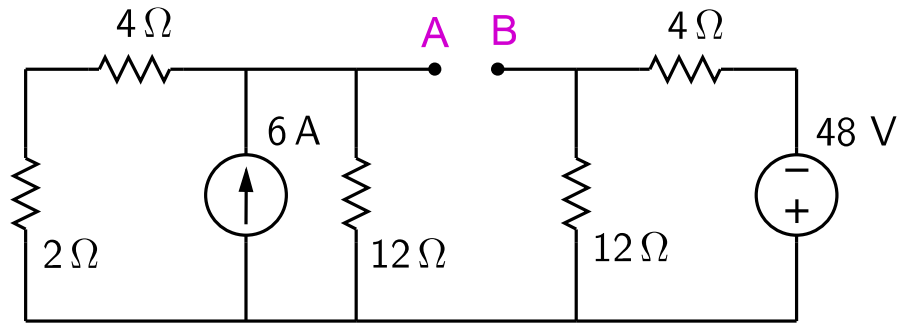

Connect a voltage source between A and B.

Plot i versus v .

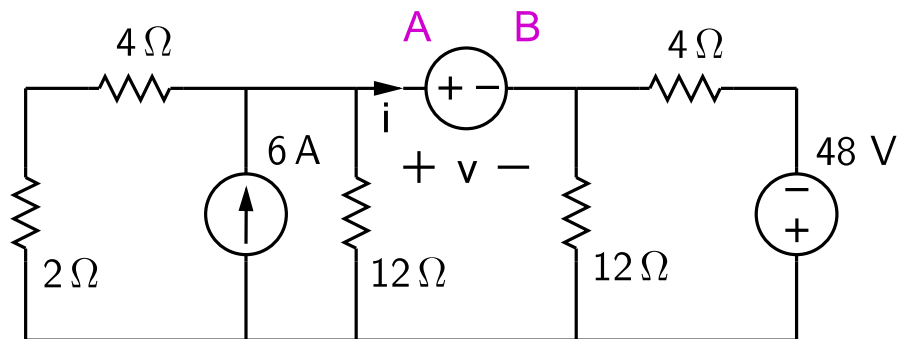


V_{oc} = intercept on the v -axis.

I_{sc} = intercept on the i -axis.


Graphical method for finding V_{Th} and R_{Th}

SEQUEL file: ee101_thevenin_1.sqproj

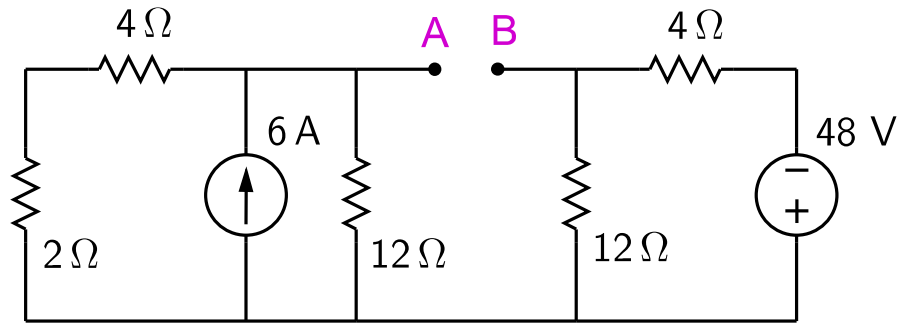


Connect a voltage source between A and B.

Plot i versus v .

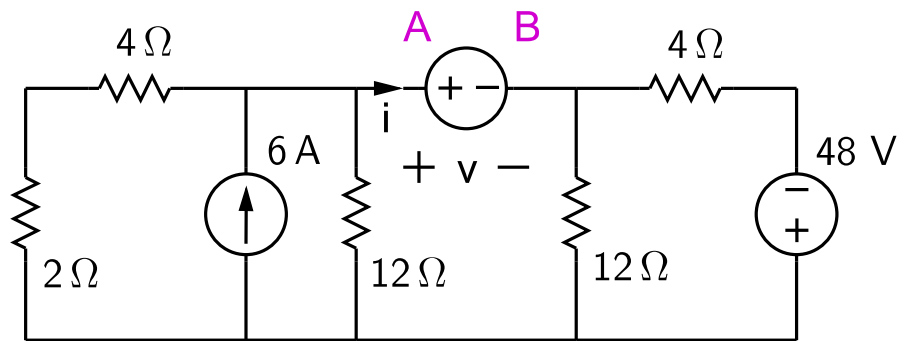


V_{oc} = intercept on the v -axis.

I_{sc} = intercept on the i -axis.

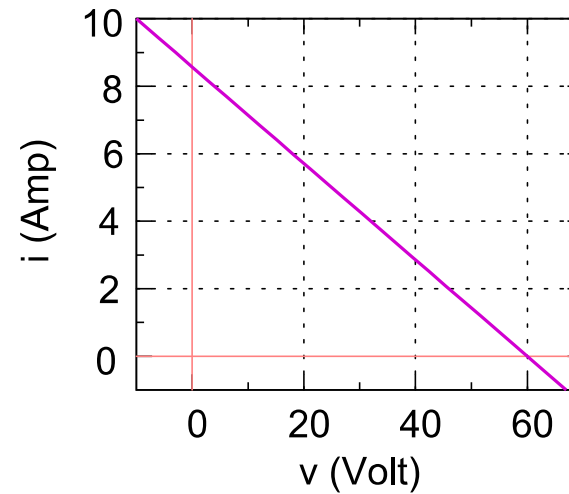


Graphical method for finding V_{Th} and R_{Th}

SEQUEL file: ee101_thevenin_1.sqproj

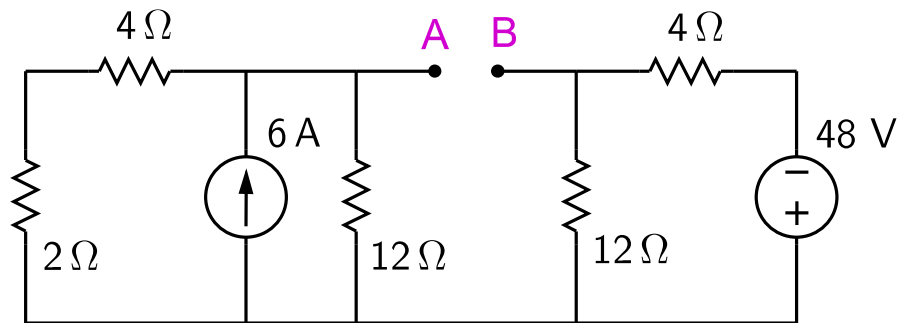


Connect a voltage source between A and B.

Plot i versus v .

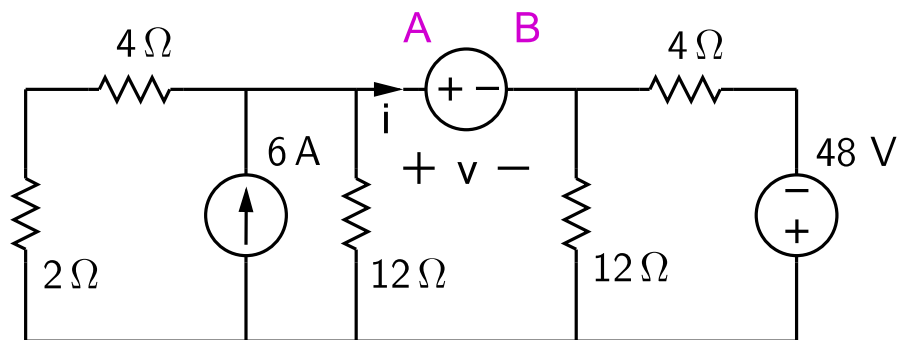

$V_{oc} =$ intercept on the v -axis.

$I_{sc} =$ intercept on the i -axis.

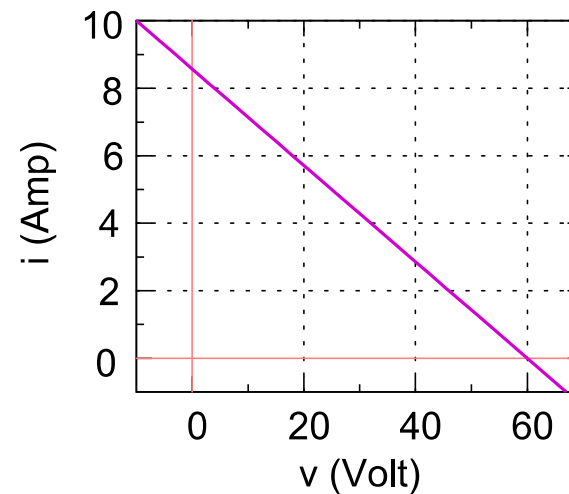


$$V_{oc} = 60\text{ V}, I_{sc} = 8.57\text{ A}$$

$$R_{Th} = V_{sc}/I_{sc} = 7\ \Omega$$


Graphical method for finding V_{Th} and R_{Th}

SEQUEL file: ee101_thevenin_1.sqproj

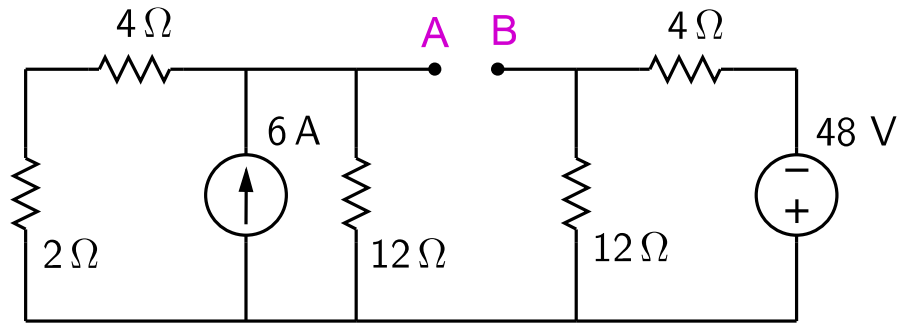


Connect a voltage source between A and B.

Plot i versus v .

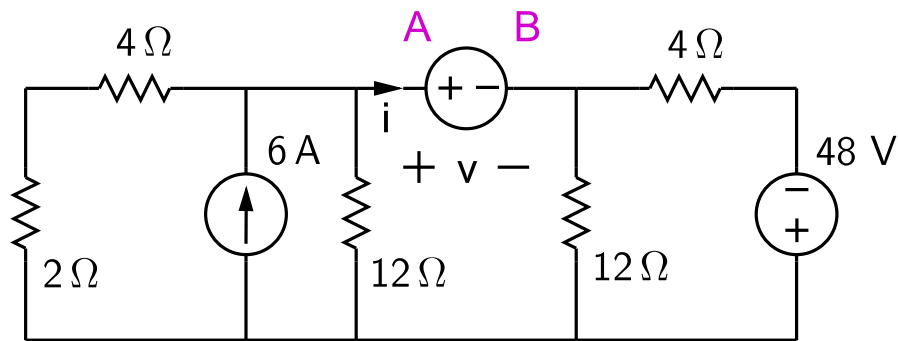

$V_{oc} =$ intercept on the v -axis.


$I_{sc} =$ intercept on the i -axis.

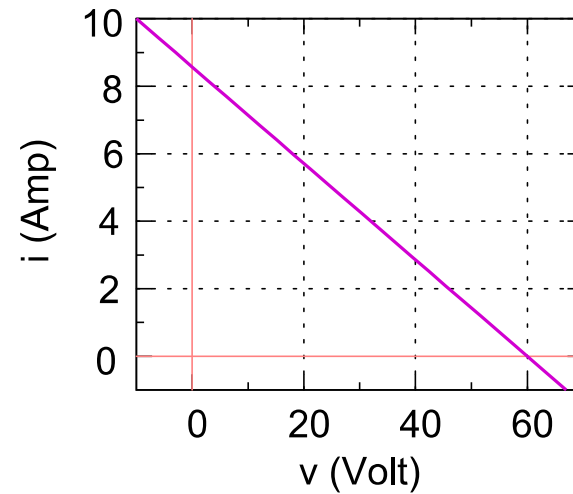


$$V_{oc} = 60\text{ V}, I_{sc} = 8.57\text{ A}$$

$$R_{Th} = V_{sc}/I_{sc} = 7\ \Omega$$

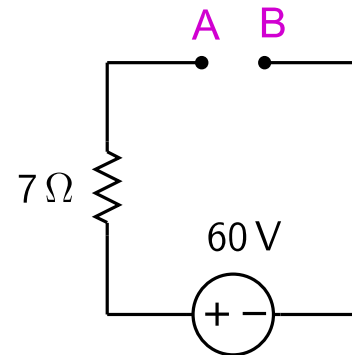
$$V_{Th} = 60\text{ V}$$
$$R_{Th} = 7\ \Omega$$




Norton equivalent circuit

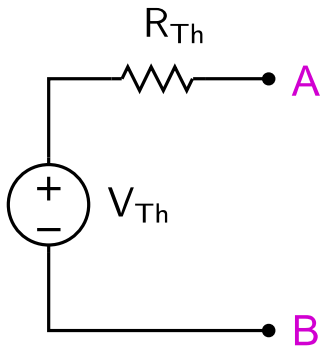

Norton equivalent circuit

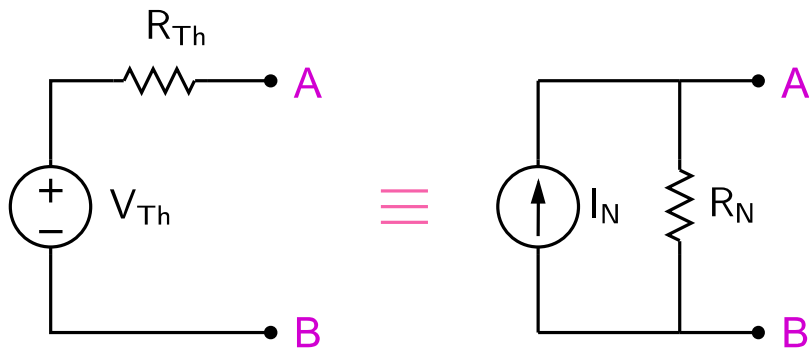


Norton equivalent circuit

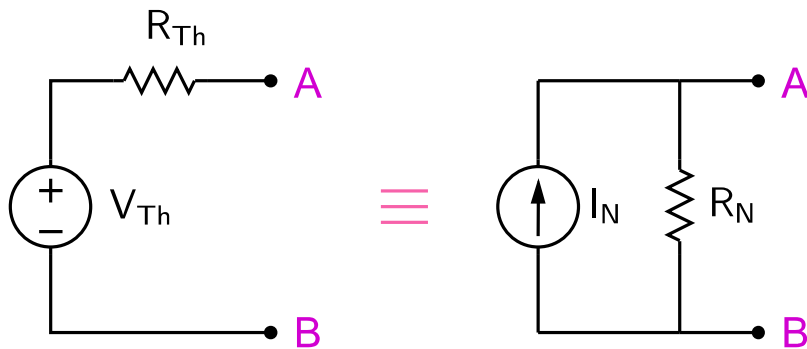

* Consider the open circuit case.


Norton equivalent circuit

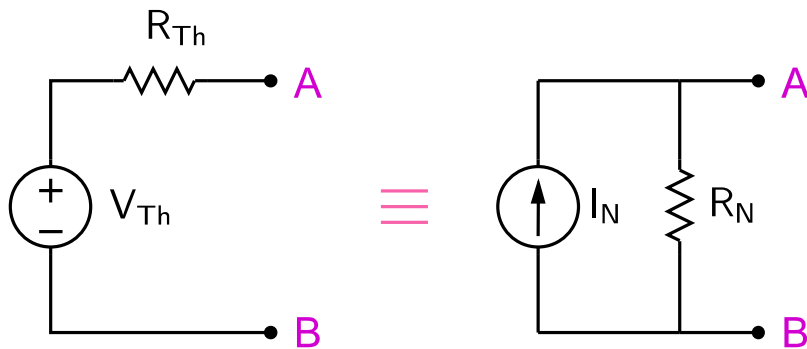

* Consider the open circuit case.

Thevenin circuit: $V_{AB} = V_{Th}$.

Norton equivalent circuit

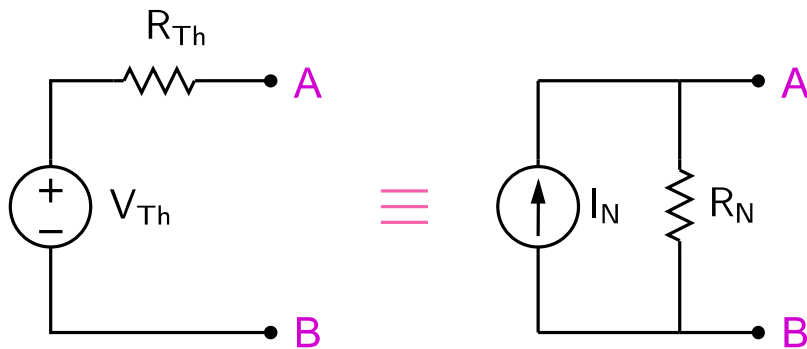


* Consider the open circuit case.

Thevenin circuit: $V_{AB} = V_{Th}$.

Norton circuit: $V_{AB} = I_N R_N$.

Norton equivalent circuit

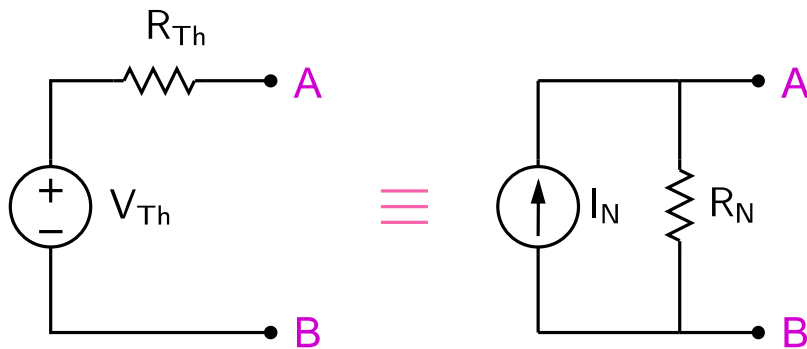


* Consider the open circuit case.

Thevenin circuit: $V_{AB} = V_{Th}$.

Norton circuit: $V_{AB} = I_N R_N$.

$\Rightarrow V_{Th} = I_N R_N$.

Norton equivalent circuit

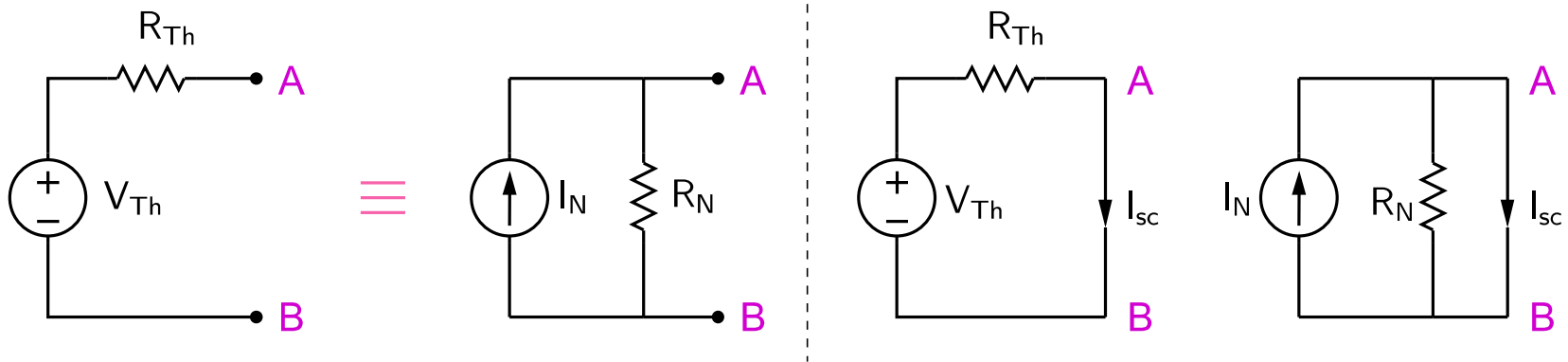

- * Consider the open circuit case.


Thevenin circuit: $V_{AB} = V_{Th}$.

Norton circuit: $V_{AB} = I_N R_N$.

$$\Rightarrow V_{Th} = I_N R_N.$$

- * Consider the short circuit case.

Norton equivalent circuit

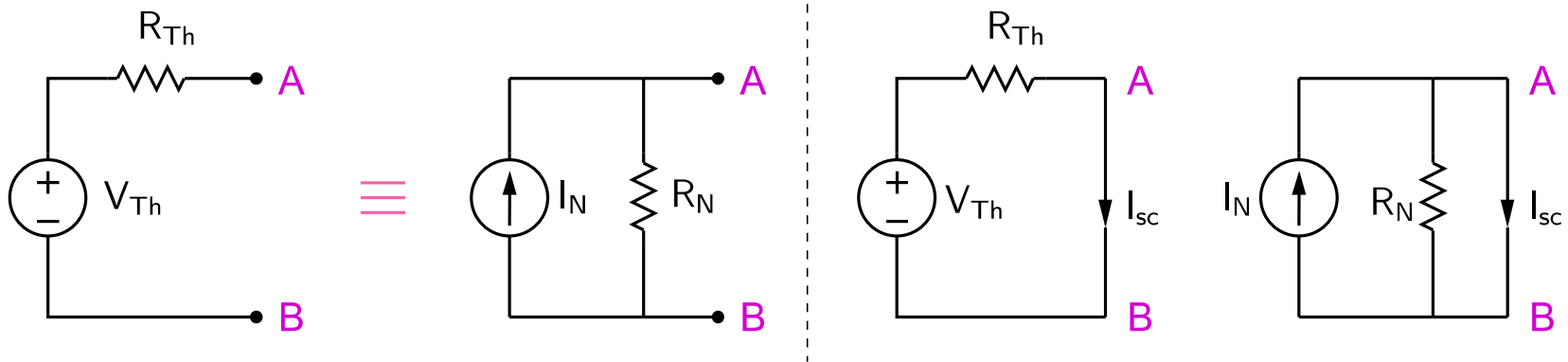

- * Consider the open circuit case.

Thevenin circuit: $V_{AB} = V_{Th}$.


Norton circuit: $V_{AB} = I_N R_N$.

$$\Rightarrow V_{Th} = I_N R_N.$$

- * Consider the short circuit case.

Thevenin circuit: $I_{sc} = V_{Th} / R_{Th}$.

Norton equivalent circuit

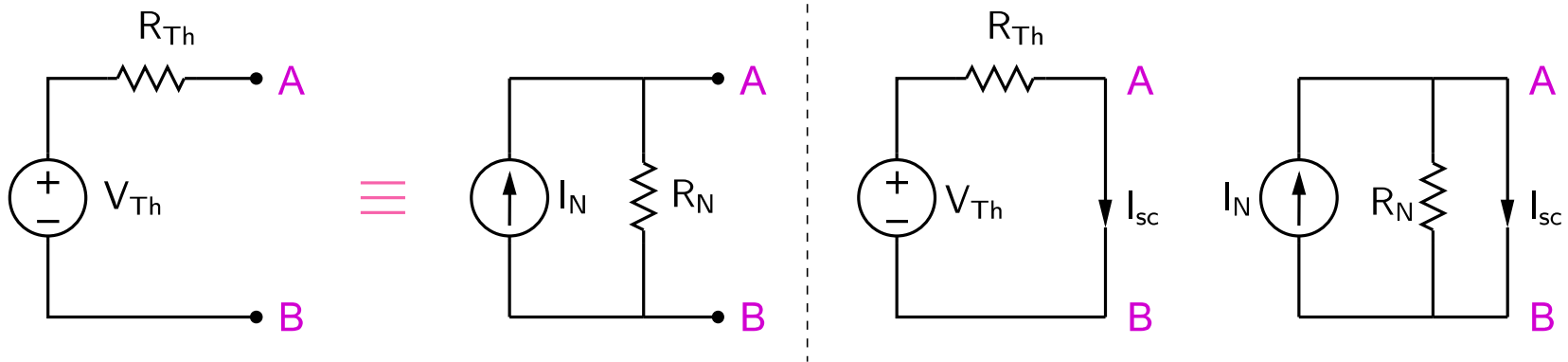

- * Consider the open circuit case.

Thevenin circuit: $V_{AB} = V_{Th}$.

Norton circuit: $V_{AB} = I_N R_N$.


$$\Rightarrow V_{Th} = I_N R_N.$$

- * Consider the short circuit case.

Thevenin circuit: $I_{sc} = V_{Th} / R_{Th}$.

Norton circuit: $I_{sc} = I_N$.

Norton equivalent circuit

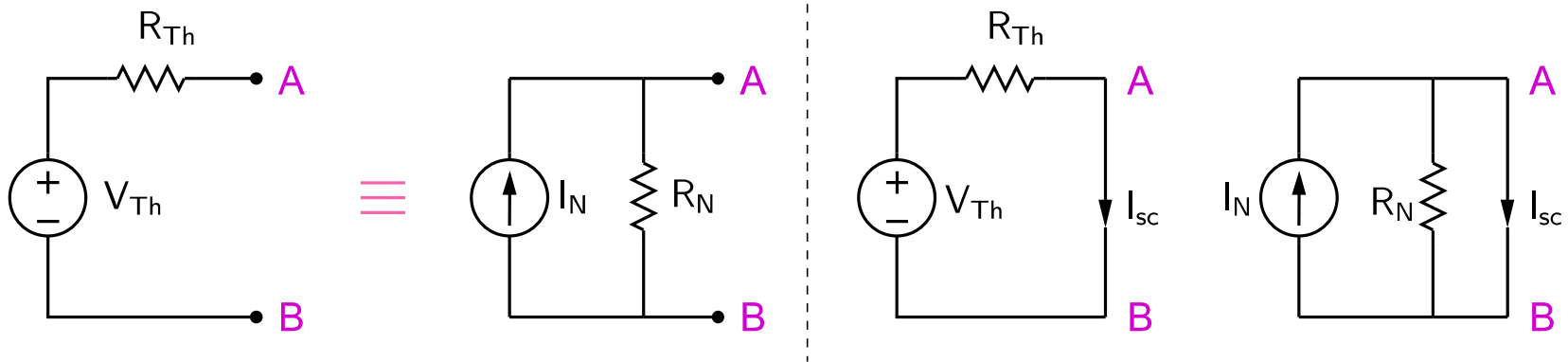

- * Consider the open circuit case.

Thevenin circuit: $V_{AB} = V_{Th}$.

Norton circuit: $V_{AB} = I_N R_N$.

$$\Rightarrow V_{Th} = I_N R_N.$$


- * Consider the short circuit case.

Thevenin circuit: $I_{sc} = V_{Th} / R_{Th}$.


Norton circuit: $I_{sc} = I_N$.

$$\Rightarrow R_{Th} = R_N.$$


Example

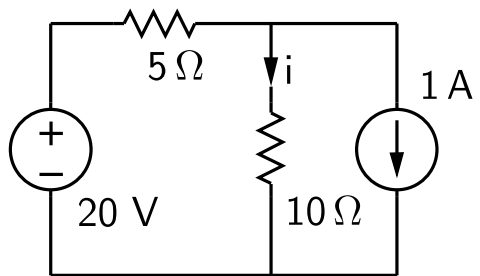

Example

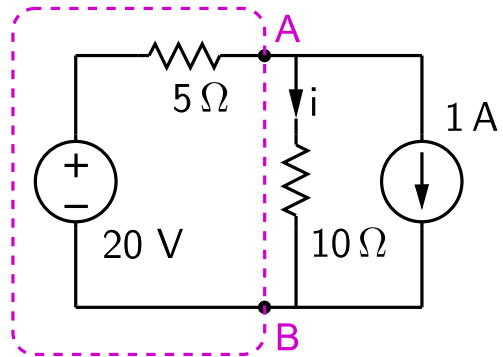


Example

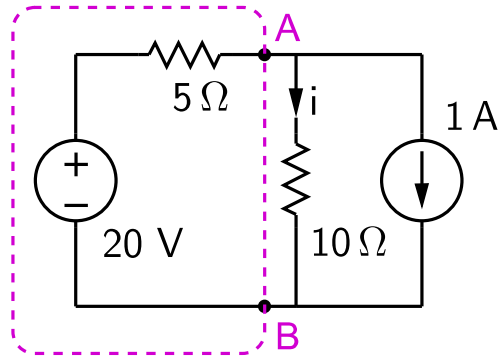

$$R_N = 5\ \Omega$$


$$I_N = \frac{20\text{ V}}{5\ \Omega} = 4\text{ A}$$

Example

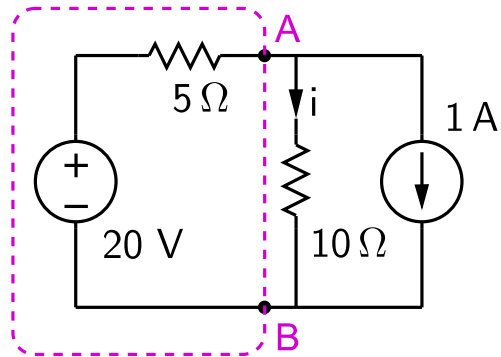


$$R_N = 5 \Omega$$
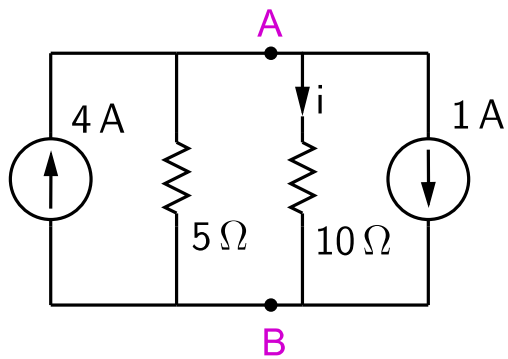
$$I_N = \frac{20 \text{ V}}{5 \Omega} = 4 \text{ A}$$





Example


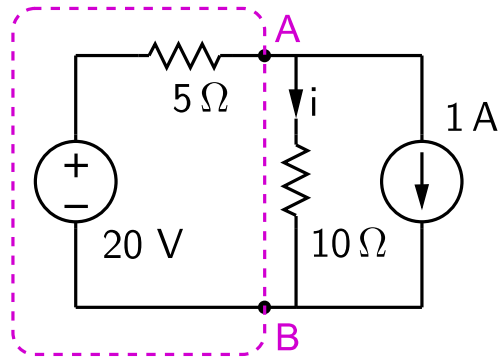


$$R_N = 5 \Omega$$
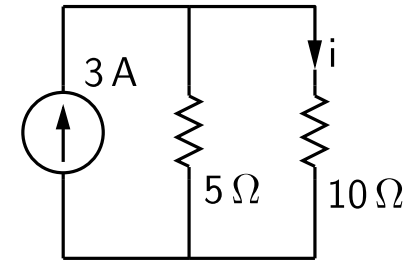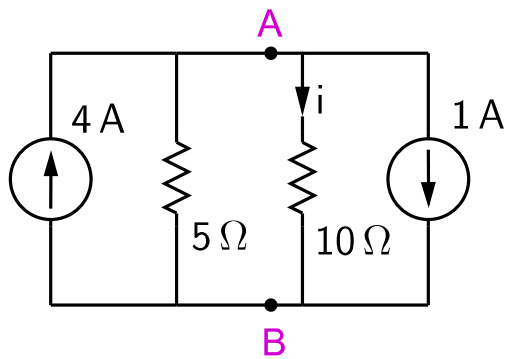
$$I_N = \frac{20 \text{ V}}{5 \Omega} = 4 \text{ A}$$





Example

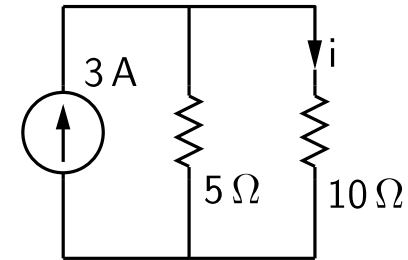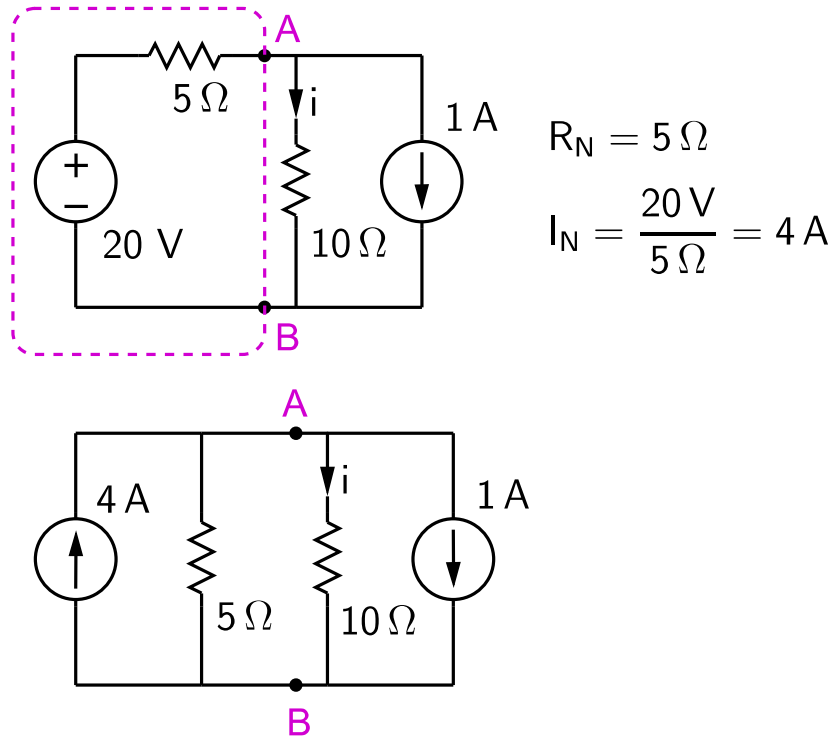

$$i = 3 \text{ A} \times \frac{5}{5 + 10}$$
$$= 1 \text{ A}$$

Example

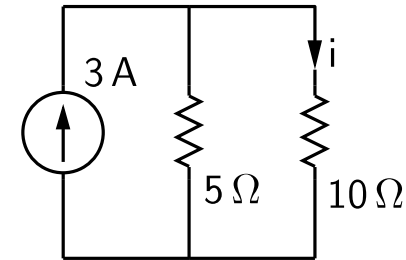
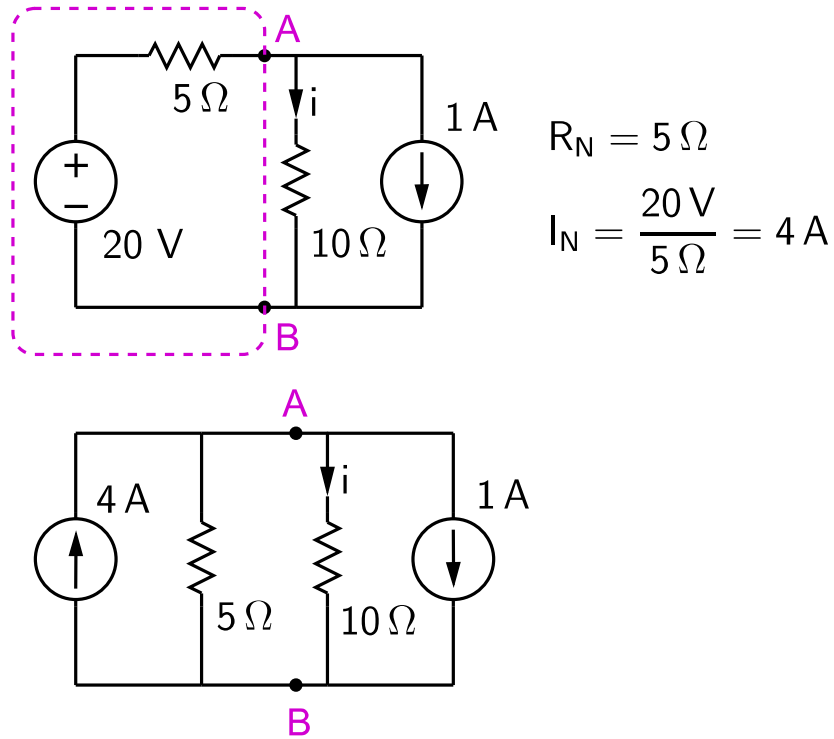


$$i = 3 \text{ A} \times \frac{5}{5 + 10}$$
$$= 1 \text{ A}$$

Home work:

* Find i by superposition and compare.

Example

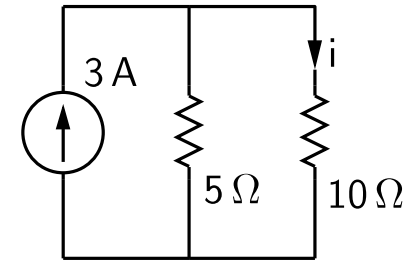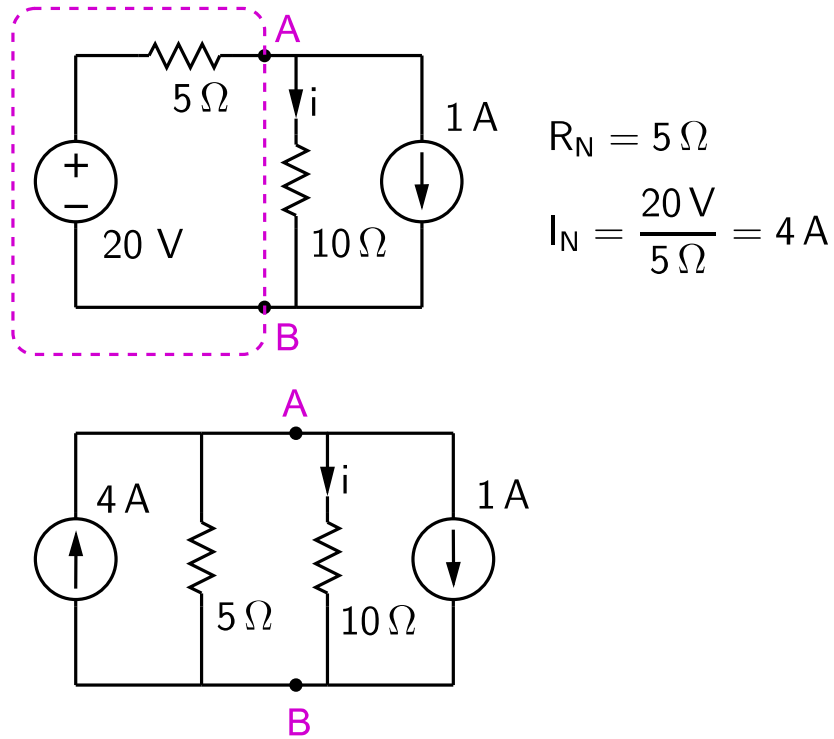

$$i = 3 \text{ A} \times \frac{5}{5 + 10}$$

$$= 1 \text{ A}$$

Home work:

- * Find i by superposition and compare.
- * Compute the power absorbed by each element, and verify that $\sum P_i = 0$.